
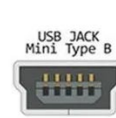




# NANO PINOUT

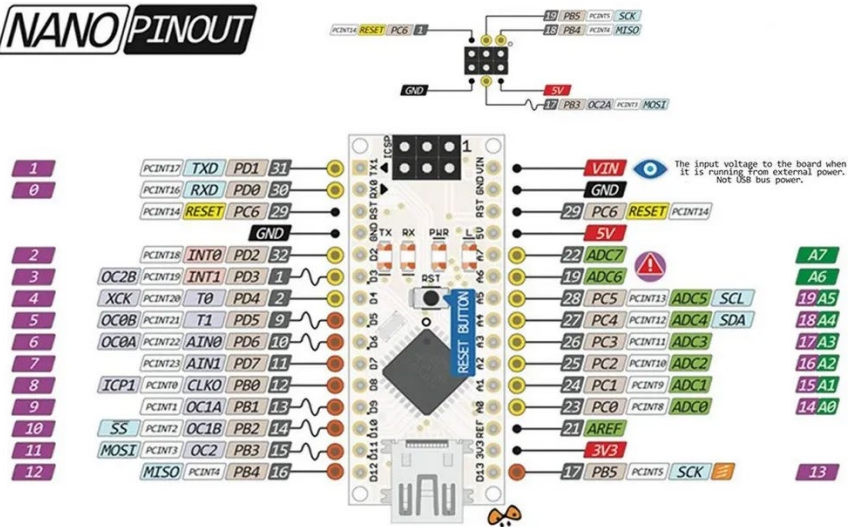

- Analog exclusively Pins
- Absolute MAX per pin 40mA recommended 20mA
- Absolute MAX 200mA for entire package

Descubrearduino.com

# NANO PINOUT

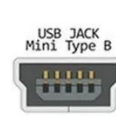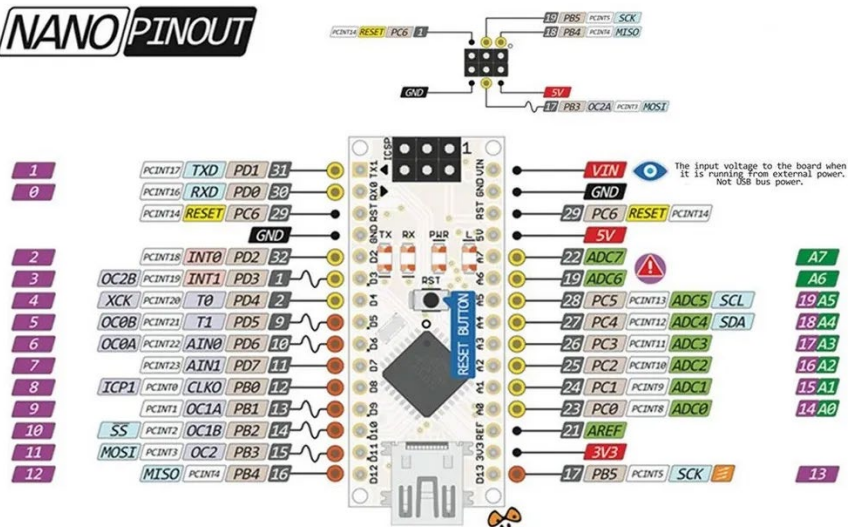

- Analog exclusively Pins
- Absolute MAX per pin 40mA recommended 20mA
- Absolute MAX 200mA for entire package


Descubrearduino.com

### LED Current Limiting Resistor:

$$V_{\text{Resistor}} = V_{\text{Supply}} - V_{F\_LED} \rightarrow V_{\text{Resistor}} = I \times R \rightarrow R = V_{\text{Resistor}} \div I$$

See **datasheet** or guess:  $I \rightarrow 3 \text{ mA}$ ,  $V_{F\_red} = 1.9 \text{ V}$ ;  $V_{F\_yel/ora} = 2.0 \text{ V}$ ;  $V_{F\_grn} = 2.1 \text{ V}$ ;  $V_{F\_blu/whi} = 3.4 \text{ V}$ ;

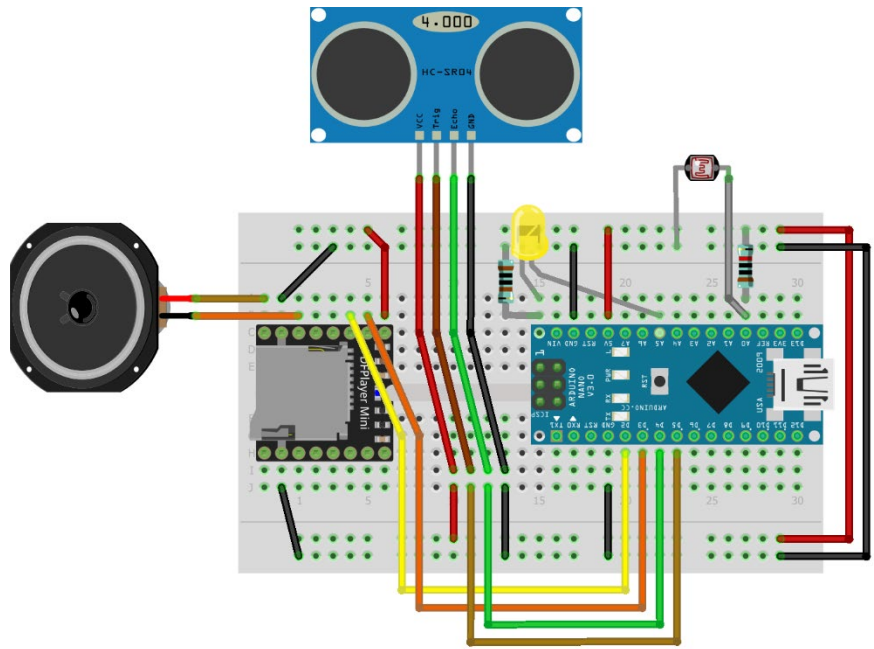Example:  $5 (V_{\text{Supply}}) - 2.0 (V_F) = 3 (V_{\text{Resistor}})$  and  $R = 3 \div 0.003 = 1 \text{ k}\Omega$




fritzing

### LED Current Limiting Resistor:

$$V_{\text{Resistor}} = V_{\text{Supply}} - V_{F\_LED} \rightarrow V_{\text{Resistor}} = I \times R \rightarrow R = V_{\text{Resistor}} \div I$$

See **datasheet** or guess:  $I \rightarrow 3 \text{ mA}$ ,  $V_{F\_red} = 1.9 \text{ V}$ ;  $V_{F\_yel/ora} = 2.0 \text{ V}$ ;  $V_{F\_grn} = 2.1 \text{ V}$ ;  $V_{F\_blu/whi} = 3.4 \text{ V}$ ;

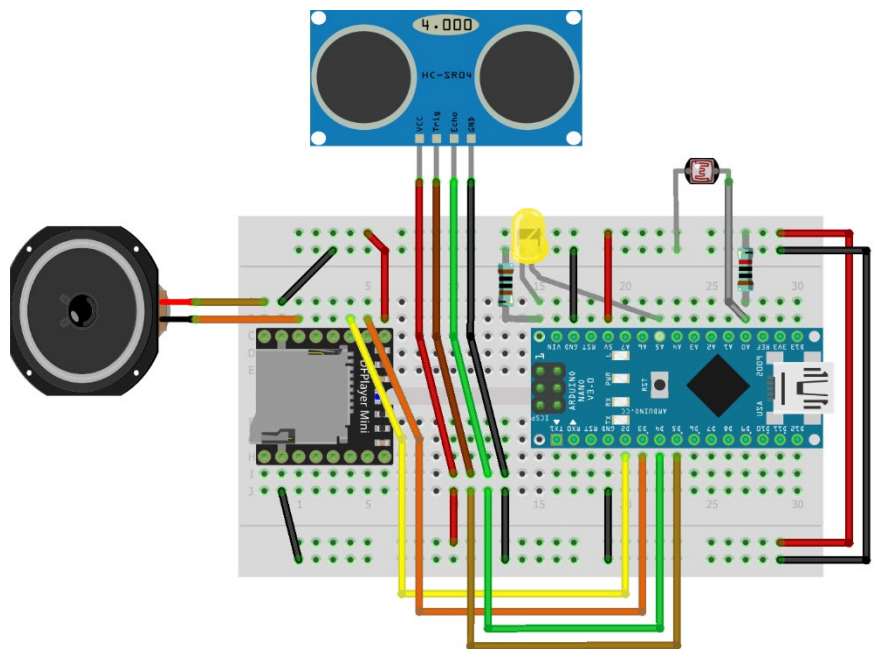Example:  $5 (V_{\text{Supply}}) - 2.0 (V_F) = 3 (V_{\text{Resistor}})$  and  $R = 3 \div 0.003 = 1 \text{ k}\Omega$



fritzing